

Contents

1	About	1
2	Amplifier - HX711	1
2.1	Amplifier schema	1
2.2	HX711 library	1
2.3	Arduino code	1
2.4	Datasheet	1
2.5	Load cell wiring	1
3	Basic load cell resistance checks	2

1 About

This is project of DIY dynameter

2 Amplifier - HX711

2.1 Amplifier schema

This is the schema for all the wiring with arduino Schema

2.2 HX711 library

You can download the necessary library here [Download](#)

2.3 Arduino code

Necessary code:

- calibration the code is here
- measurement the code is here

2.4 Datasheet

[link](#)

2.5 Load cell wiring

Not important

HX711	Load cell
E+	white
E-	red
S+	black
S-	green

3 Basic load cell resistance checks

Resistance check	Typical 350 Ω
Ex+ to Ex-	$\sim 410\Omega$
S+ to S-	350Ω
Ex+ to S+	$\sim 315\Omega$
Ex+ to S-	$\sim 315\Omega$
Ex- to S+	$\sim 280\Omega$
Ex- to S-	$\sim 280\Omega$